 


Flip-flops & Registers


S-R Flip-flop - data storage circuit



Function table

set	Reset	Q	\bar{Q}
0	0	Hold condition	
0	1	Flip-flop reset	
1	0	Flip-flop set	
1	1	Not used	

Gated S-R Flip-flop

 


If gate = 0, set-reset is disabled & output was the previous output.
If gate = 1 set-reset is read

Async = Output immediately to input changes

Sync = Operates sequentially with control input. (like the gate input / clock)

Gated D-Flip-flop

 

D-Latch : To be latched means for the output to follow the previous output after the gate or clock input goes to low.